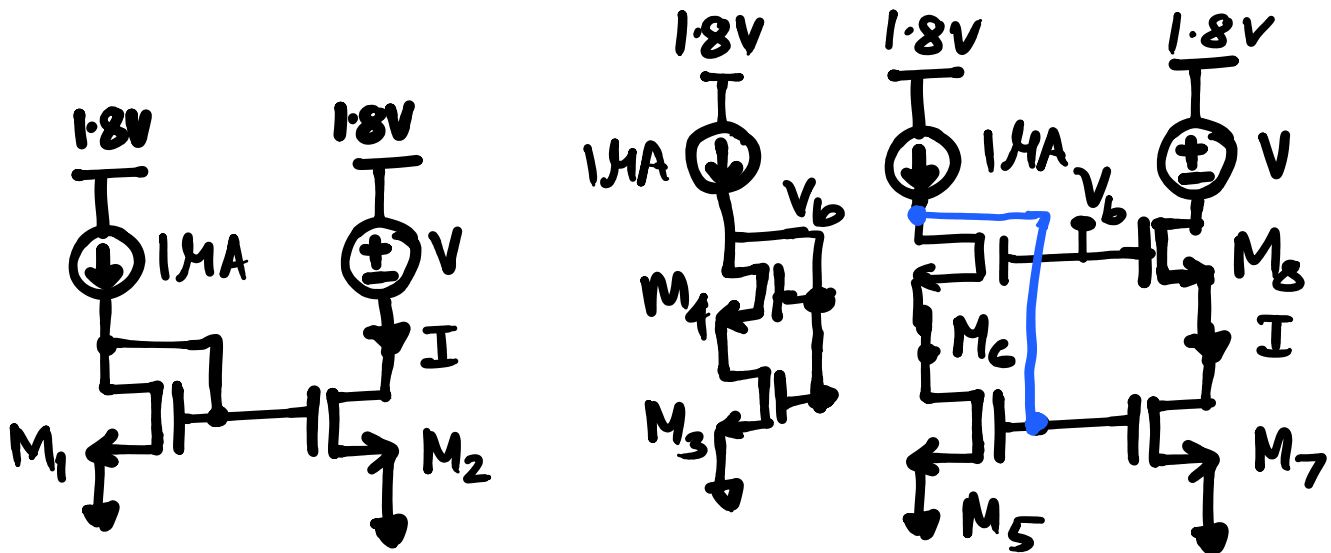


## Assignment-2



In the above circuits all transistor except  $M_3$  are identical.  $M_3$  has  $W = 0.24\mu$  and  $L = 5\mu$ .

For all other transistors choose  $W = 2\mu$  &  $L = 0.18\mu$

- ① Plot  $I$  as  $V$  is varied from 0 to 1.8V
- ② Now change  $L$  of device  $M_{1,2,4,5,6,7,8}$  to  $1\mu$  from  $0.18\mu$  and redo the part (a)

(3 Marks)

Q.2 Design a common source amplifier with DC Gain = 30dB and  $U_{GB} = 50\text{MHz}$ . Minimize the power dissipation. Report all operating points. show its AC magnitude & phase response. (4 Marks)

Q.3 Perform noise simulation of your designed amplifier and calculate its input referred voltage squared noise voltage in 1MHz BW. Compare it with analytical expression discussed in the class.